



MAASAI MARA UNIVERSITY

REGULAR UNIVERSITY EXAMINATIONS

2018/2019 ACADEMIC YEAR

SECOND YEAR SECOND SEMESTER

SCHOOL OF SCIENCE

BACHELOR OF SCIENCE IN PHYSICS

COURSE CODE: PHY 2212

COURSE TITLE: LABORATORY IV

DATE:

TIME:

INSTRUCTIONS TO CANDIDATES

- Answer Question **ONE** and any other **TWO**.
- Use of sketch diagrams where necessary and brief illustrations are encouraged.
- Read the instructions on the answer booklet keenly and adhere to them.

*This paper consists of **seven** printed pages. Please turn over.*

QUESTION ONE [COMPULSORY] (20 MARKS)

Consider figure 1 below.

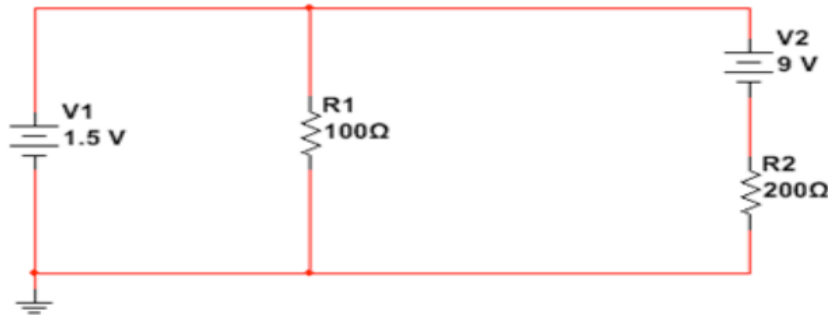


Figure 1

Kirchhoff's Current Law states that the current entering a point in a circuit is equal to the summation of the currents exiting. Kirchhoff's Voltage Law states that the summation of all voltage drops in a closed loop must equal to zero which is a result of the electrostatic field being conservative. (Conventional) current flowing through the cell has a positive voltage (gains energy) whereas current going through a resistor has a negative voltage (loses energy). This information is simplified in figure 2.

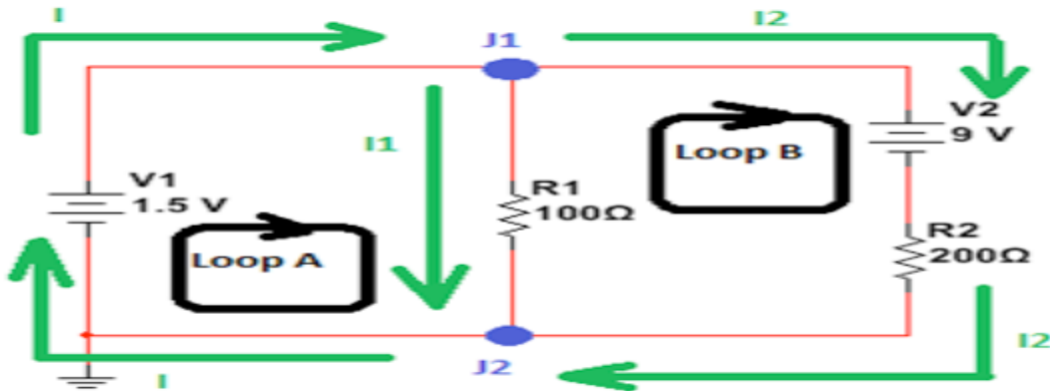


Figure 2

- a) Express the current I in terms of I_1 and I_2 **(1 mark)**
- b) Use the Kirchhoff's Laws described above to solve for the following;
 - a) (i) I_1 **(2 marks)**
 - (ii) I_2 **(3 marks)**

(iii) I (1 mark)

b) Determine the voltage drops V_{R1} and V_{R2} across each resistor

(i) V_{R1} (1 mark)

(ii) V_{R2} (1 mark)

c) You are required to implement the above circuit during a practical session.

(i) Re-sketch the diagram illustrating how you should configure the DMM to measure voltage across R_1 and R_2 (2 marks)

(ii) Re-sketch the diagram illustrating how you should configure the DMM to measure current through R_1 and R_2 (2 marks)

(iii) State **two** precautions that you should observe in this experiment (2 marks)

(iv) State **two** sources of error in this experiment and how each can be mitigated (4 marks)

(d) State one application of the circuits represented in figure 1 (1mark)

QUESTION TWO (10 MARKS)

The following is part of a student's report of an experiment to investigate the variation of current I with potential difference V for a semiconductor diode. "I put the diode in forward bias as shown in the circuit diagram. I increased the potential difference across the diode until a current flowed. I measured the current flowing for different values of the potential difference. I recorded the following data."

V(V)	0.60	0.64	0.68	0.72	0.76	0.80
I (mA)	2	4	10	18	35	120

(a) What was wrong with the student's report? (1 mark)

(b) Draw a circuit diagram used by the student. (2 marks)

- (c) Plot a graph of I_D against V_D to show how the current varies with the potential difference. **(4 marks)**
- (d) Estimate from your graph the junction voltage of the diode. **(1 mark)**
- (e) The student then put the diode in reverse bias and repeated the experiment. What changes did the student make to the initial circuit? **(2 marks)**

QUESTION THREE (10 MARKS)

Consider the electrical schematic drawing shown in figure 3 below.

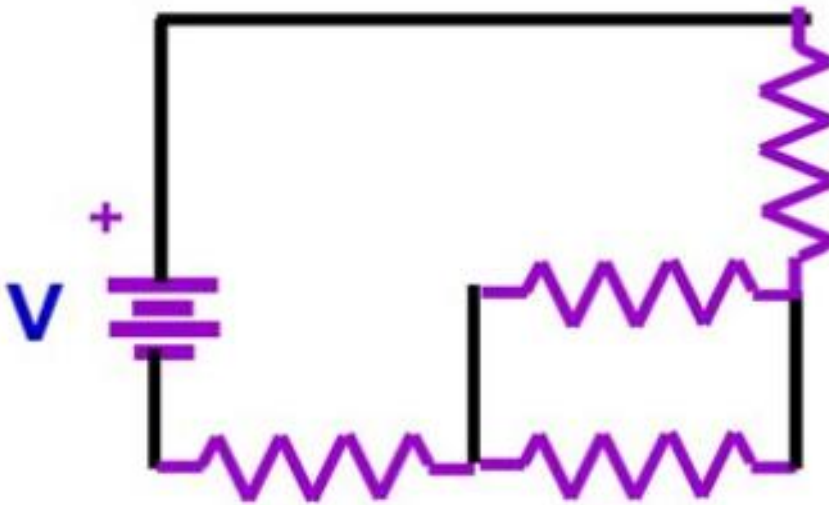


Figure 3

- (a) On the breadboard (figure 5), show how the electrical circuit corresponding to the above schematic drawing should appear. Assume all resistors have the same resistance R and that the power supply has a potential difference V . **(5 marks)**
- (b) Express the current flowing through the entire circuit in terms of V and R only. **(5 marks)**

QUESTION FOUR (10 MARKS)

The circuit in figure 4 below shows four light-emitting diodes connected to a resistor R and a 6 V a.c. supply of frequency 1 Hz.

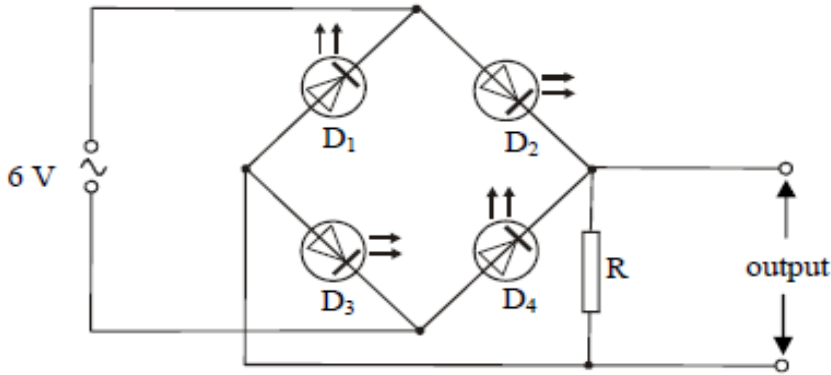


Figure 4

- (a) Which was the likely aim of this experiment? **(1 mark)**
- (b) What is observed when the circuit is operating? **(2 marks)**
- (c) What is observed when the frequency of the a.c. supply is increased to 50 Hz? **(1 mark)**
- (d) Give **one** function of the resistor R **(1 mark)**
- (e) How was the output voltage displayed? **(1 mark)**
- (f) Draw graphs to show the differences between the input voltage and the output voltage. **(3 marks)**
- (g) It is noticed that the output voltage is lower than the input voltage. Explain why. **(1 mark)**

CANDIDATE'S REG. NUMBER:.....

After answering on figure 5, detach this page and insert in your answer booklet

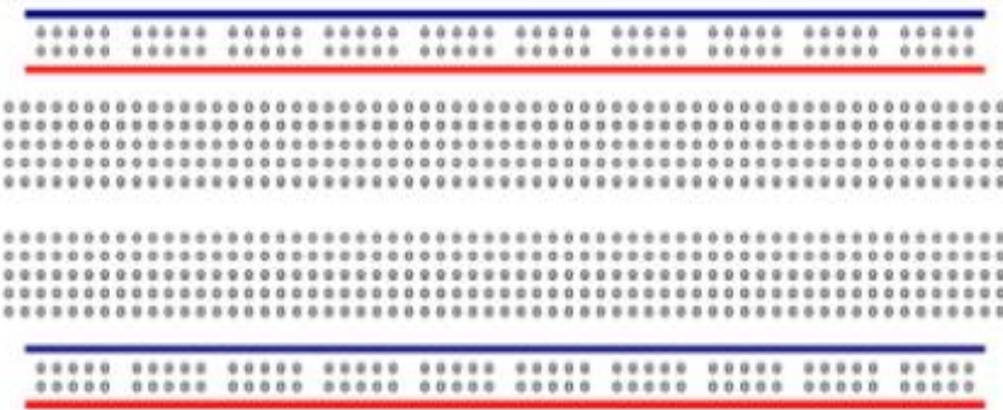


Figure 5

CANDIDATE'S REG. NUMBER:.....

*Plot the graph **only** on this sheet and do your calculations in the answer booklet! After answering, detach this page and insert in your answer booklet*

