



MAASAI MARA UNIVERSITY

REGULAR UNIVERSITY EXAMINATIONS

2022/2023 ACADEMIC YEAR

FIRST YEAR SECOND SEMESTER

**SCHOOL OF PURE, APPLIED AND HEALTHY
SCIENCES**

**MASTER OF SCIENCE IN PHYSICS
(ELECTRONICS)**

COURSE CODE: PHY 8210

COURSE TITLE: INTEGRATED ELECTRONICS

DATE: 19/4/2023

TIME: 1100-1400 HRS

INSTRUCTIONS TO CANDIDATES

1. Answer Question **ONE** and any other **Two** questions

*This paper consists of **four** printed pages. Please turn over.*

Question one [30 Marks]

- (a) Define the following terms [5marks]
- i. Noise
 - ii. 555 timers
 - iii. An analog circuit
 - iv. An active filter
 - v. An instrumentation amplifier
- (b) Draw a circuit diagram of a basic diode-based log amplifier. [4marks]
- (c) Explain the main drawback of the analog circuits. [2marks]
- (d) Draw a well labelled circuit of basic Sample-and-Hold amplifier. [4marks]
- (e) State three applications of a high-speed analog-to-digital converter. [3marks]
- (f) Differentiate between digital to analog converters and analog to digital converters. [4marks]
- (g) State four analog physical quantities found in nature. [4marks]
- (h) State and explain two sources of electronic noise. [4marks]

QUESTION TWO [20 MARKS]

- (a). (i) State two examples of digital computer circuits [2marks]
(ii) Discuss the operation of a digital circuit. [4marks]
- (b) Explain two advantages of digital circuit over analog circuit. [4marks]
- (c) State and explain three differences between analog and digital circuits. [6marks]
- (d) With suitable circuit diagrams, differentiate between a low pass filter and a high pass filter [4marks]

QUESTION THREE [20MARKS]

- (a) Explain two advantages of a binary system [4marks]
- (b) Draw a well-labelled diagram of:
- (i) the block diagram of a counter-ramp and a successive approximation A–D converter. [4marks]
 - (ii) the analog waveforms in a counter-ramp A–D converter. [3marks]

(iii) the analog waveforms in a successive approximation A–D converter. [3marks]

(c) Describe the operation of an analog comparators. [4marks]

(d) Differentiate between neural systems and fuzzy logic systems [2marks]

QUESTION FOUR [20MARKS]

(a) Find the network function V_2 / V_1 in the circuits shown in Fig.

(i) 1 (a) [3marks]

(ii) 1 (b) [3marks]

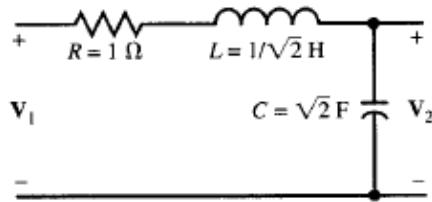


Fig 1 (a)

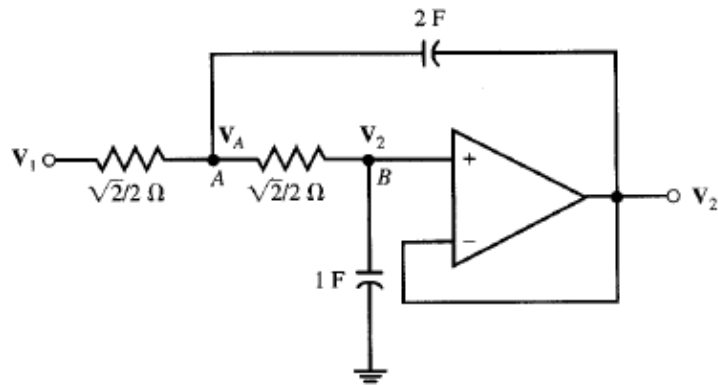


Fig. 1 (b)

(b) State and explain the successive approximation A–D converter [4marks]

(c) Discuss two applications of DACs and ADCs [4marks]

(d) Draw a block diagram of a triangular wave generator. Explain how it works. [4marks]

(e) State two noncomputer applications of digital circuits [2marks]

QUESTION FIVE [20MARKS]

(a) Draw a circuit diagram of a Schmitt trigger [3marks]

(b) What is an Analog comparator? Explain its working principle. [5marks]

(c) A sample of Si is doped with 10^{16} phosphorus atoms/cm³. Find the Hall voltage in the sample with $W=500 \mu\text{m}$, $A=2.5 \times 10^{-3} \text{cm}^2$, $I=1 \text{mA}$, and $B_z=10^{-4} \text{Wb/cm}^2$. [4marks]

(d) Briefly explain the basic operation of a Sample and Hold Amplifier. [4marks]

(e) Explain two advantages of implementing a lock–in amplifier using digital technologies [4marks]